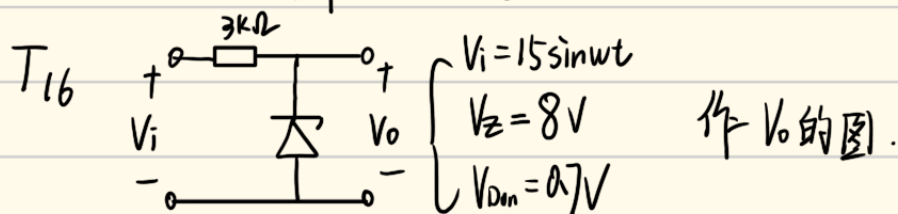


线性电子线路 2025-2026 期末 A 卷 回忆版.


15 选择. 多做往年有惊喜. 并没有 E/E 增益 DE 增益问题; 差分计算没考大题出了 3 个选择.

推荐 1 小时定时完成.

8 道大题, 今年作图题多.



T17

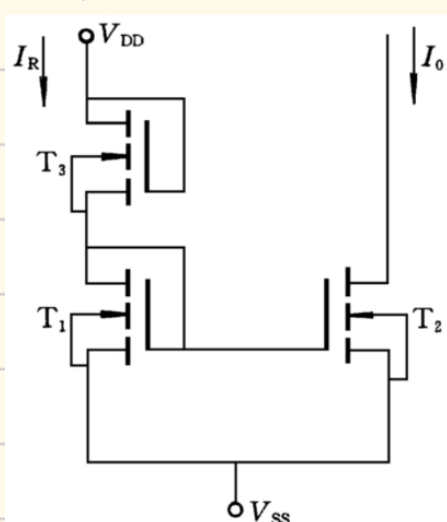



T_1, T_2, T_3 参数一样

$V_{DD} = 6V$
 $V_{GS(th)} = 1.5V$
 $I_0 = 3\mu A$
 $\frac{\mu C}{2} = 0.05 \mu A/V^2$

求 $\frac{v_o}{v_i}$.

T18 写. 反馈类型和极性

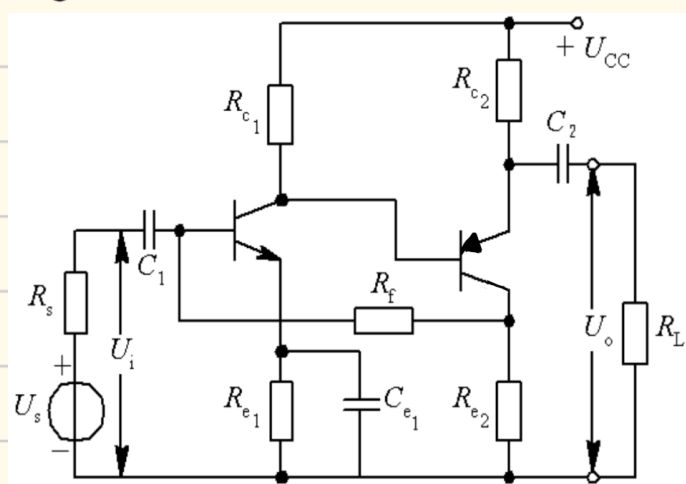

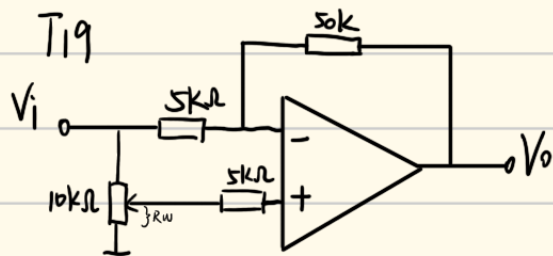


$R_W = k \cdot 10k\Omega \quad k \in [0,1]$

求增益范围.

分析此电路. 你

T20

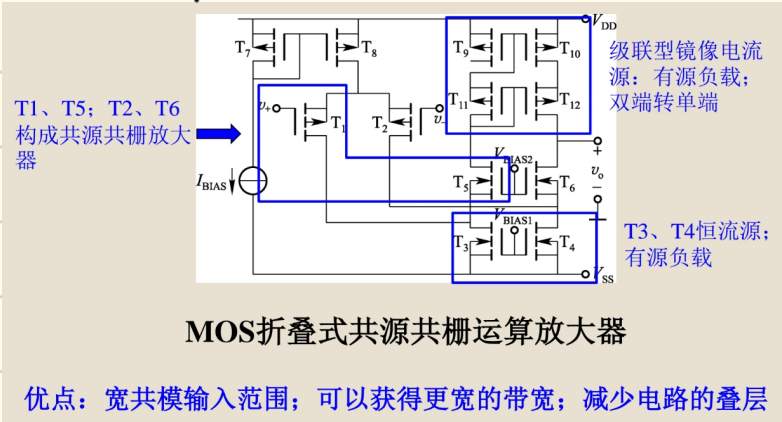


T21 $A(j\omega) = \frac{10^{13}(j\omega + 100)}{(j\omega + 10^6)(j\omega + 10^7)}$

- (1) 波特图.
(2) 中频增益; 上限频率.

T22

(就是9A)

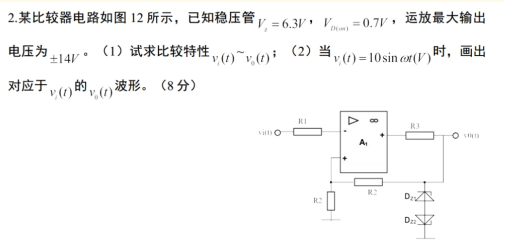

T23 $g_m = 1\text{mS}$ $r_{ds} = 4\text{k}\Omega$

求 (1) 交流通路; 小信号电路模型
(2) A_v R_o R_i

